

浙江大学

计算机组成实验报告

实验名称: ALU、Regfiles 以及有限状态机设计

姓 名: 蒋奕

学 号: 3210103803


专 业: 计算机科学与技术


课程名称: 计算机组成

实验地点: 东 4-509


指导老师: 赵莎

2023 年 3 月 9 日

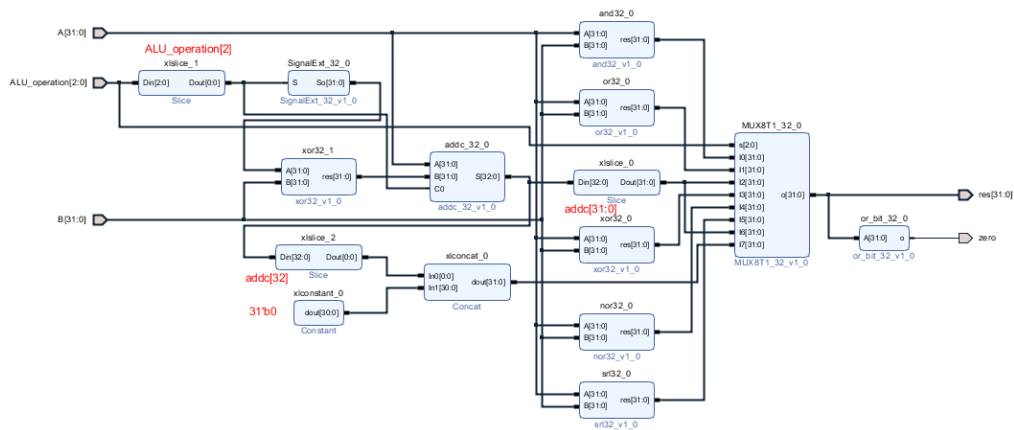


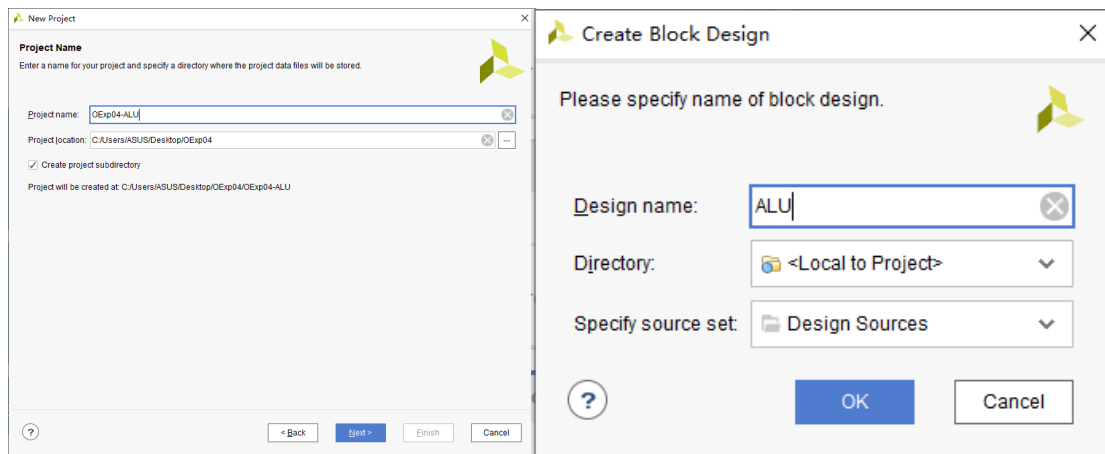

生成 IP 并且封装：

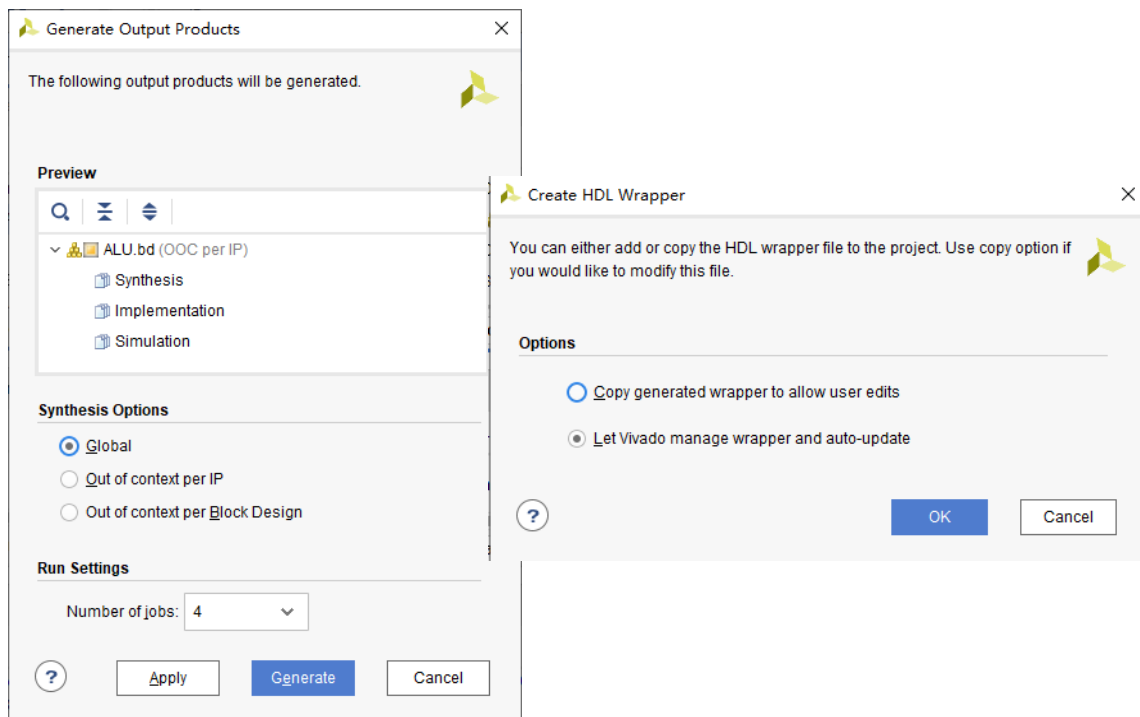

建立仿真文件仿真：

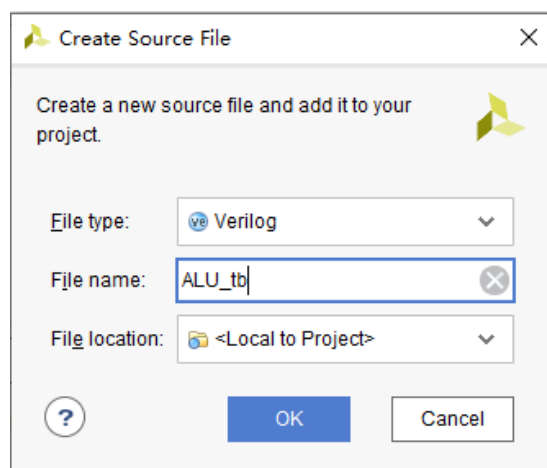

2. 设计实现数据通路部件 Register Files：采用硬件描述语言的设计方法

实现 $32 \times 32\text{bit}$ 寄存器组

优化逻辑实验 Regs，行为描述并仿真结果

Regfile 封装关键点：

①端口警告原因是 clk 端口属性未知

点击 clk 进入端口编辑界面,Parameters 下添加 ASSOCIATED_BUSIF, 然后在新建的 ASSOCIATED_BUSIF 这个参数后面的 value 列输入定义的时钟信号的名字, 此处为 clk

②复位信号自动反向原因是系统默认是低电平而实验设计时高电平, 需要进行属性约束

点击 rst 进入端口编辑界面,Parameters 下添加 POLARITY。然后在新建的 POLARITY 这个参数后面的 value 列输入属性 ACTIVE_HIGH。

注意：后续封装的含时钟和复位信号的 IP，建议均作此类属性限制以免设计时产生问题

3. 设计有限状态机完成序列检测器并测试

状态机设计方法：

一段式描述（即状态跳转与输出信号都在同一个 always 块里面进行描述）

二段式描述（即将输出信号与状态跳转分开描述，便于设计代码管理）

三段式描述（即将输出信号与状态跳转分开描述，并且状态跳转用组合逻辑来控制）

设计要求：

用状态机设计序列检测器（1110010-----序列检测器）


设计功能：

设计一个序列检测器 检测的序列为 1110010。

当输入信号 X 依次为 1110010 时 输出信号 Y 输出一个高电平否则输出信号 Y 为低电平。

时序图：

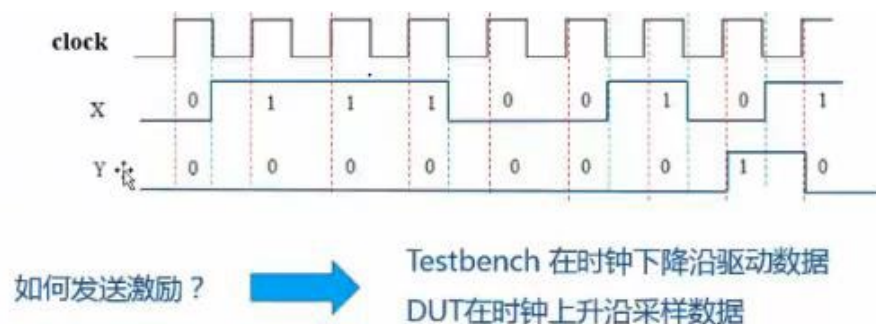序列检测器是一种同步时序电路它用于搜索检测输入的二进制代码串中是否出现指定的代码序列 1110010 序列。检测原理图如下：




2.2 实验原理

1. ALU 功能:

| ALU Control Lines | Function | note |
|-------------------|------------------|------|
| 000 | And | 兼容 |
| 001 | Or | 兼容 |
| 010 | Add | 兼容 |
| 110 | Sub | 兼容 |
| 111 | Set on less than | |
| 100 | nor | 扩展 |
| 101 | srl | 扩展 |
| 011 | xor | 扩展 |

原理图:

 

2. Reg file 端口

二个读端口:

Rs1_addr;Rs1_data


Rs2_addr;Rs2_data

一个写端口，带写信号

Wt_addr;Wt_data

RegWrite

示意图：

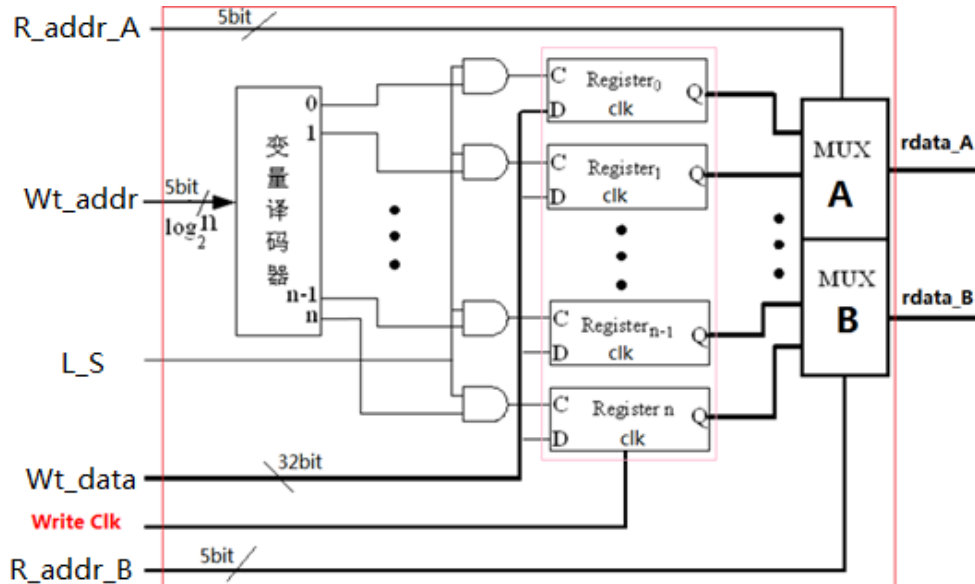


3. 状态机

系统架构和接口定义

| 接口 | 接口定义 |
|-------|------|
| clk | 系统时钟 |
| rst_n | 系统复位 |
| X | 序列输入 |
| Y | 检测输出 |

状态转换图：

 


三、 实验设备和环境

1. 计算机（Intel Core i5 以上，4GB 内存以上）系统
2. Sword2.0/Sword4.0 开发板
3. Xilinx VIVADO 2017.4 及以上开发工具

四、 实验实现方法、步骤与调试

1. ALU

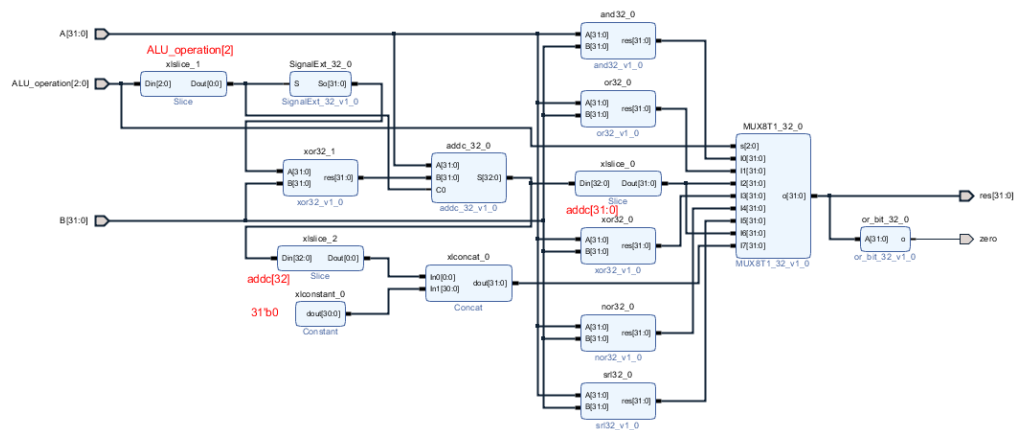

2. Reg file 代码

```
module regs(  
    input clk , rst , RegWrite ,  
    input [4:0] Rs1_addr, Rs2_addr,Wt_addr ,  
    input [31:0] Wt_data,  
    output [31:0] Rs1_data, Rs2_data  
);  
    reg [31:0] register [1:31]; // r1 r31  
    integer i;  
    assign Rs1_data = (Rs1_addr== 0) ? 0 : register[Rs1_addr]; //  
read rdata_A  
    assign Rs2_data = (Rs2_addr== 0) ? 0 : register[Rs2_addr]; //  
read rdata_B  
    always @(posedge clk or posedge rst )  
    begin if (rst ==1)  
        for (i=1; i<32; i=i+1) register[i] <= 0; // reset  
        else if ( ( Wt_addr != 0) && (RegWrite == 1) )  
            register[Wt_addr] <= Wt_data ; // write  
    end  
endmodule
```

3. 有限状态机代码

```
module seq_moore(  
    input clk,input reset,input in,output out  
);  
    //define state  
    parameter [2:0] S0 = 3'b000, S1 = 3'b001, S2 = 3'b010, S3 = 3'b011,  
                    S4 = 3'b100, S5 = 3'b101, S6 = 3'b110, S7 = 3'b111;  
    reg [2:0] curr_state; reg [2:0] next_state; //internal variable  
    always @(posedge clk or negedge reset) //first segment:state transfer  
    begin  
        if(!reset)// reset == 0  
            curr_state <= S0;  
        else  
            curr_state <= next_state;  
        end  
    always @(curr_state or in) //second segment:transfer condition  
    begin  
        case(curr_state)  
            S0:begin  
                if(in==0) next_state = S0;  
                else next_state = S1;  
            end  
            S1:begin  
                if(in==0) next_state = S0;  
                else next_state = S2;  
            end  
            S2:begin  
                if(in==0) next_state = S0;  
                else next_state = S3;  
            end  
            S3:begin  
                if(in==0) next_state = S4;  
                else next_state = S3;  
            end  
            S4:begin  
                if(in==0) next_state = S5;  
                else next_state = S1;  
            end  
            S5:begin  
                if(in==0) next_state = S0;  
                else next_state = S6;  
            end  
            S6:begin  
                if(in==0) next_state = S7;  
            end  
        endcase  
    end  
end
```




```

        else next_state = S2;
    end
    S7:begin
        if(in==0) next_state = S0;
        else next_state = S1;
    end
    default next_state = S0;
endcase
end
//three segment: state output
//moore type fsm
    assign out = (curr_state == S7) ? 1 : 0;
endmodule

```

五、 实验结果与分析

1. ALU

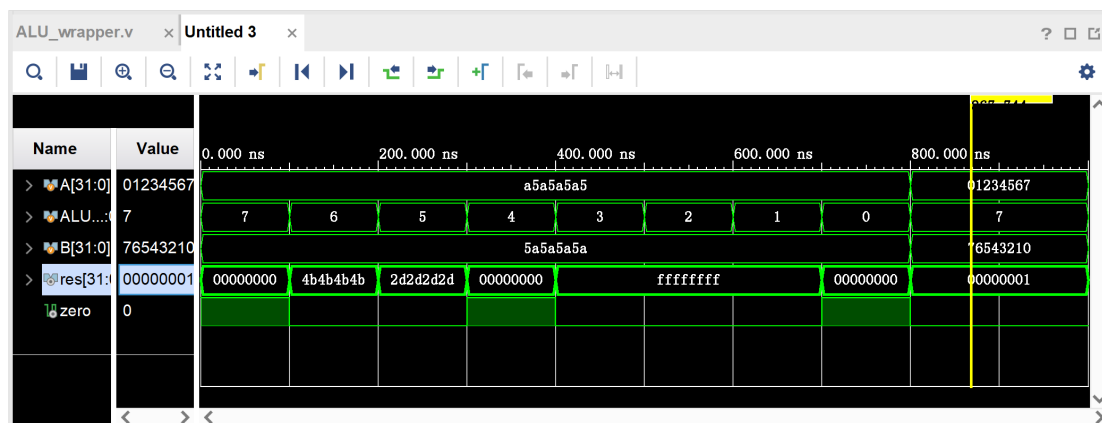

仿真代码:

```

module ALU_tb;
    reg [31:0] A;
    reg [2:0] ALU_operation;
    reg [31:0] B;
    wire [31:0] res;
    wire zero;
    ALU_wrapper ALU_wrapper_U(
        .A(A),
        .B(B),
        .ALU_operation(ALU_operation),
        .res(res),
        .zero(zero)
    );

```


```

initial begin
    A = 32'hA5A5A5A5;
    B = 32'h5A5A5A5A;
    ALU_operation = 3'b111;
    #100;
    ALU_operation = 3'b110;
    #100;
    ALU_operation = 3'b101;
    #100;
    ALU_operation = 3'b100;
    #100;
    ALU_operation = 3'b011;
    #100;
    ALU_operation = 3'b010;
    #100;
    ALU_operation = 3'b001;
    #100;
    ALU_operation = 3'b000;
    #100;
    A = 32'h01234567;
    B = 32'h76543210;
    ALU_operation = 3'b111;

end
endmodule

```

2.register file

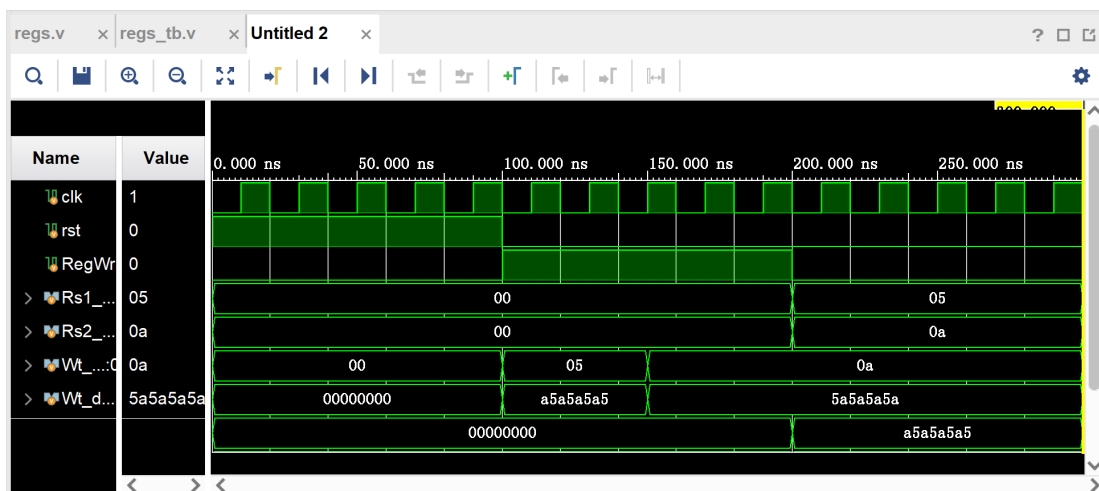


仿真代码:

```

module regs_tb;
    reg clk , rst , RegWrite;
    reg [4:0] Rs1_addr, Rs2_addr,Wt_addr;
    reg [31:0] Wt_data;
    wire [31:0] Rs1_data, Rs2_data;
    regs regs_tb_U(
        .clk(clk),
        .rst(rst),
        .RegWrite(RegWrite),
        .Rs1_addr(Rs1_addr),
        .Rs2_addr(Rs2_addr),
        .Wt_addr(Wt_addr),
        .Wt_data(Wt_data),
        .Rs1_data(Rs1_data),
        .Rs2_data(Rs2_data)
    );
    always #10 clk = ~clk;
    initial begin
        clk = 0;
        rst = 1; RegWrite = 0;
        Rs1_addr = 0; Rs2_addr = 0; Wt_addr = 0;
        Wt_data = 0;
        #100;//initial
        rst = 0;RegWrite = 1;
        Wt_addr = 5'b00101;
        Wt_data = 32'ha5a5a5a5;
        #50;
        Wt_addr = 5'b01010;
        Wt_data = 32'h5a5a5a5a;
        #50;
        RegWrite = 0;
        Rs1_addr = 5'b00101;
        Rs2_addr = 5'b01010;
        #100;
        $finish;
    end
endmodule

```

3. 有限状态机

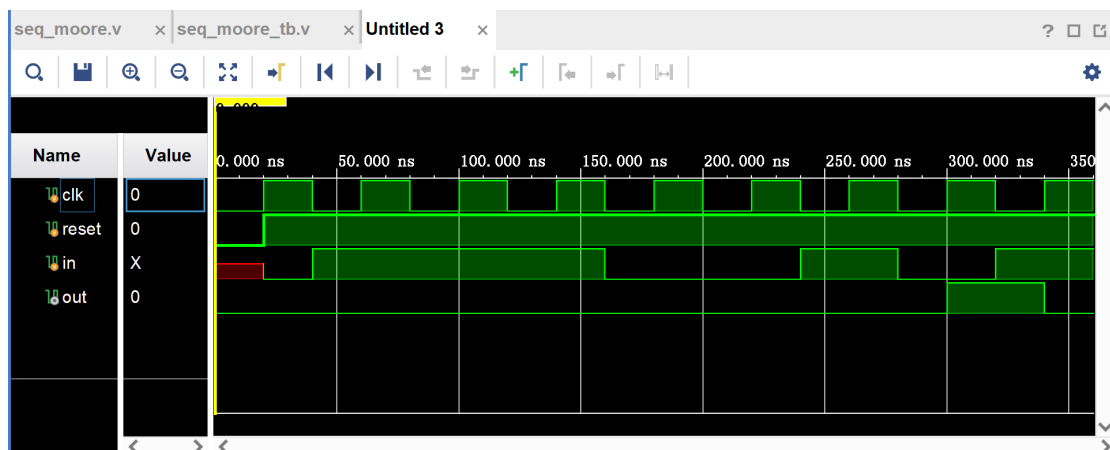

仿真代码:

```
module seq_moore_tb;
    reg clk,reset,in;
    wire out;
    always #20 clk = ~clk;
    initial begin
        clk = 0; reset = 0;#20
        reset = 1; in = 0; #20
        in = 1;#40
        in = 1; #40
        in = 1; #40
        in = 0;
        #40
        in = 0;
        #40
        in = 1;
        #40
        in = 0;
        #40
        in = 1;
        #40
        $finish;
    end
    seq_moore seq_moore_U(
        .clk(clk),
        .reset(reset),
        .in(in),
        .out(out)
    );
endmodule
```

六、 实验讨论、心得

这次实验让我充分体会到了 ALU 的原理和有限状态机的实现